

Computer-Aided VLSI System Design

Chap.4-1 Architecture Improvement of Timing, Area, and Power

Lecturer: 孫振庭 (Brian)

Graduate Institute of Electronics Engineering, National Taiwan University



NTU GIEE




Outline

- ❖ Introduction
- ❖ Register Timing
- ❖ Timing Improvements
 - Pipeline
 - Retiming
 - Parallel
- ❖ Area and Power



Introduction to Hardware Performance

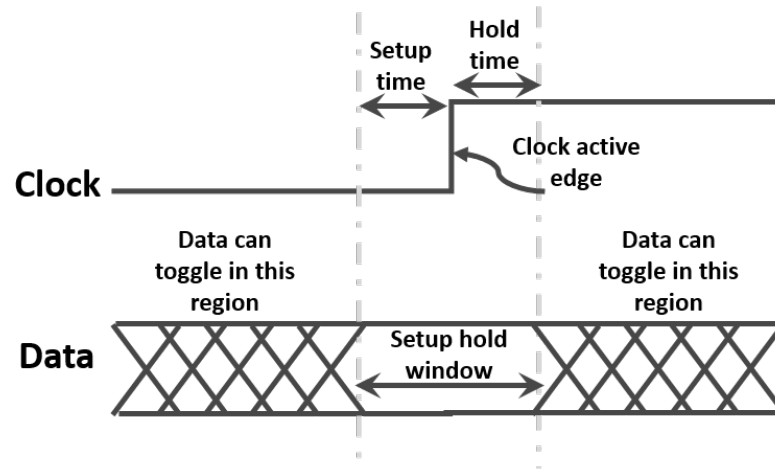- ❖ Designers should be aware of common **performance metrics**
 - Timing
 - Area
 - Power
- ❖ **Meeting timing requirements is the fundamental goal**
 - A digital circuit may not work if it has **timing violations**
 - Optimize area and power only after timing is met





Performance Optimization

❖ Limitation of synthesis tools

- Cannot automatically infer hardware constraints (e.g. clock speed, input/output delay)
- Cannot resolve all timing, area, and power issues

❖ Performance optimization is done better at the algorithmic and architecture level

- Cannot rely on synthesis tool all the time
- Plan and analyze your design for better performance



Latency and Throughput


❖ Latency

- The *time* taken to complete an operation
- e.g. cycles, seconds

❖ Throughput

- The *rate* of operations being completed
- e.g. OP/cycle, x-bit width/seconds)

❖ Example

 

- **Latency:** 3 cycles, or 30 ns
- **Throughput:** 2 OP/cycle, 100 Mb/s, or 200 MOPS



Timing Requirements

- ❖ To meet throughput requirements in system specifications, the clock cycle must be smaller than some values
- ❖ The design must meet timing **with margin**, and use **worst-case library** model in synthesis
- ❖ If the design cannot deliver certain throughput in post-synthesis simulation, we need to improve timing with the methods below:
 - Pipeline
 - Retiming
 - Parallel





Outline

- ❖ Introduction
- ❖ Register Timing
- ❖ Timing Improvements
 - Pipeline
 - Retiming
 - Parallel
- ❖ Area and Power



Register Architecture



❖ Positive edge-triggered D flip-flop

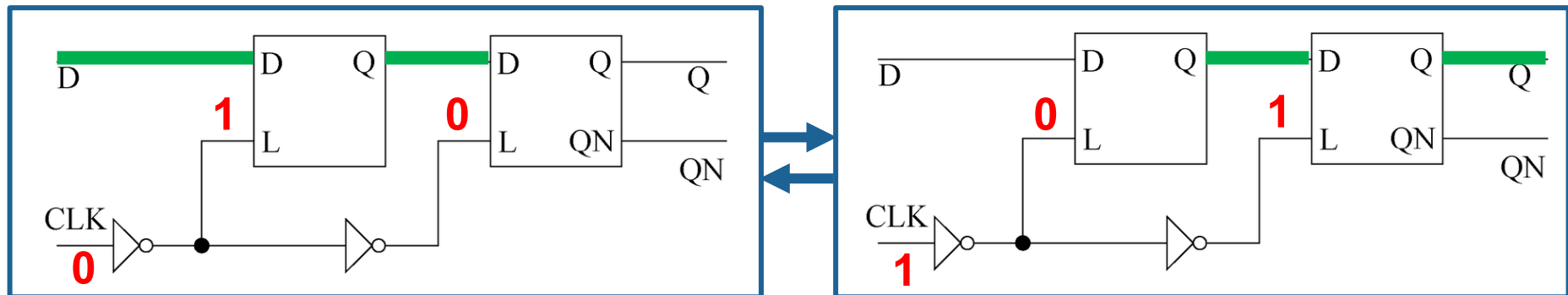 



Register Timing: Notation (1/2)



Name	Definition
t_{pd}	Logic propagation delay (maximum logic delay)
t_{cd}	Logic contamination delay (minimum logic delay)

  




Register Timing: Notation (2/2)

Name	Definition
t_{pcq}	Clock-to-Q propagation delay (maximum clk-Q delay)
t_{ccq}	Clock-to-Q contamination delay (minimum clk-Q delay)
t_{setup}	Setup time (D must be stable for t_{setup} before posedge clock)
t_{hold}	Hold time (D must be stable for t_{hold} after posedge clock)
T_c	Clock period

  



Register Timing: Max Delay

 

Requirement:



$$t_{pd} \leq T_c - \underbrace{(t_{\text{setup}} + t_{pcq})}_{\text{sequencing overhead}}$$

Setup time violation:

$$T_c - t_{pd} - t_{pcq} < t_{\text{setup}}$$



Register Timing: Min Delay

  

Requirement:

$$t_{cd} \geq t_{hold} - t_{ccq}$$


Hold time violation:

$$t_{cd} + t_{ccq} < t_{hold}$$



Calculate Register Timing

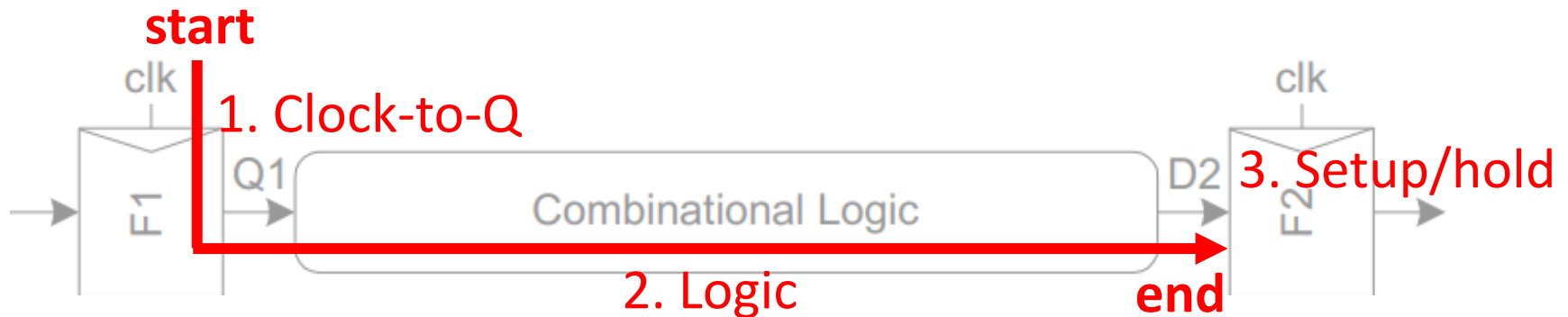- ❖ Note: register timing calculation starts from the **clock** signal





Timing Violations

❖ **Slack** should be non-negative, otherwise it is a timing violation

- Setup slack : $T_c - t_{pd} - t_{pcq} - t_{setup}$
- Hold slack : $t_{cd} + t_{ccq} - t_{hold}$

❖ **Fixing setup time violation**

1. Larger T_c (lower frequency)
2. Lower t_{pd} (pipelining, retiming)

❖ **Fixing hold time violation**

1. Larger t_{cd}
- **Note:** hold time violation cannot be fixed by adjusting T_c



Outline

- ❖ Introduction
- ❖ Register Timing
- ❖ Timing Improvements
 - Pipeline
 - Retiming
 - Parallel
- ❖ Area and Power






Improve Timing in a Design (1/2)

- ❖ **Pipelining:** exploits **temporal** parallelism
 - Insert pipeline registers without changing functionality
 - Shorter critical path -> faster achievable clock
 - Trade off latency (in cycles) to improve throughput

- ❖ **Parallelizing:** exploits **spatial** parallelism
 - Duplicate function units, works in parallel
 - With slower clock : achieve same throughput
 - With same clock : achieve higher throughput
 - Trade off area to improve throughput



Improve Timing in a Design (2/2)

 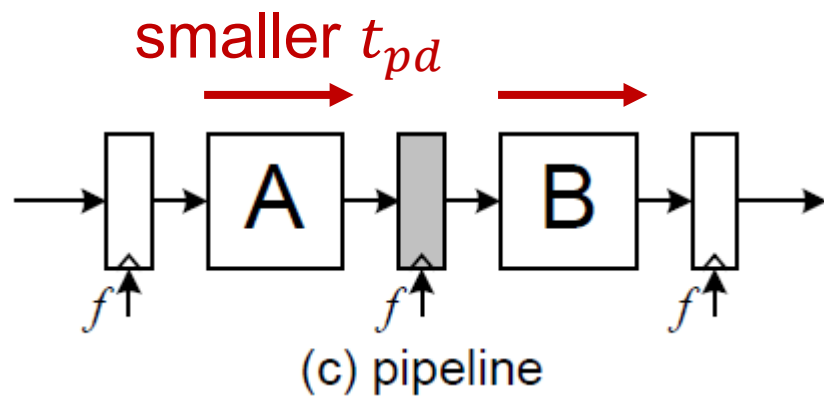 




Outline

- ❖ Introduction
- ❖ Register Timing
- ❖ Timing Improvements
 - Pipeline
 - Retiming
 - Parallel
- ❖ Area and Power




Pipelining (1/2)

❖ Original

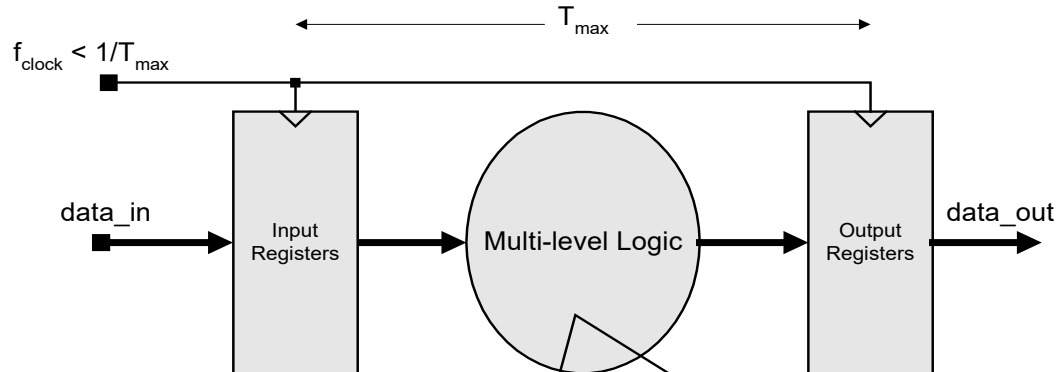


❖ 2-stage pipelining

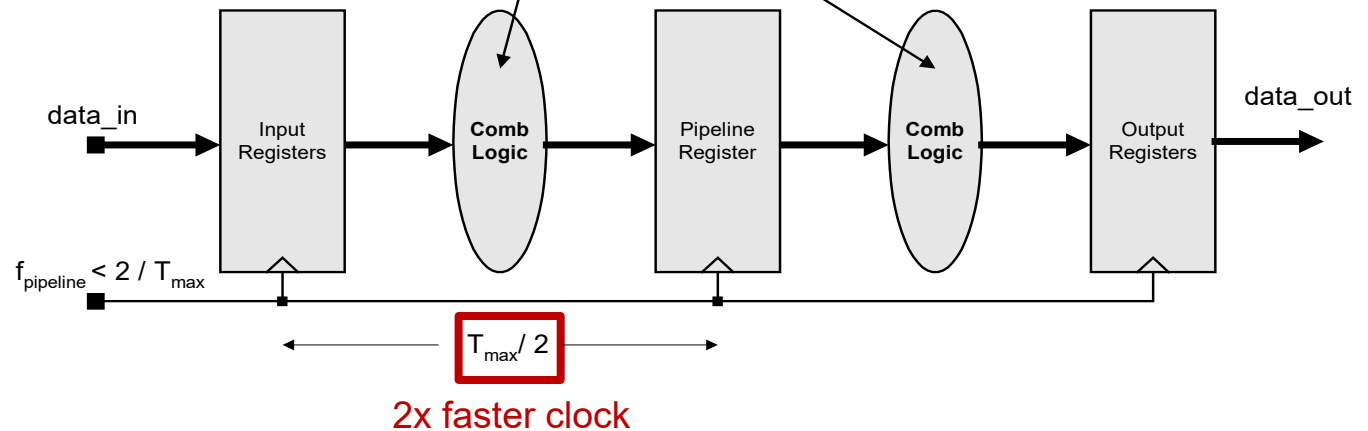




Pipelining (2/2)

❖ Original

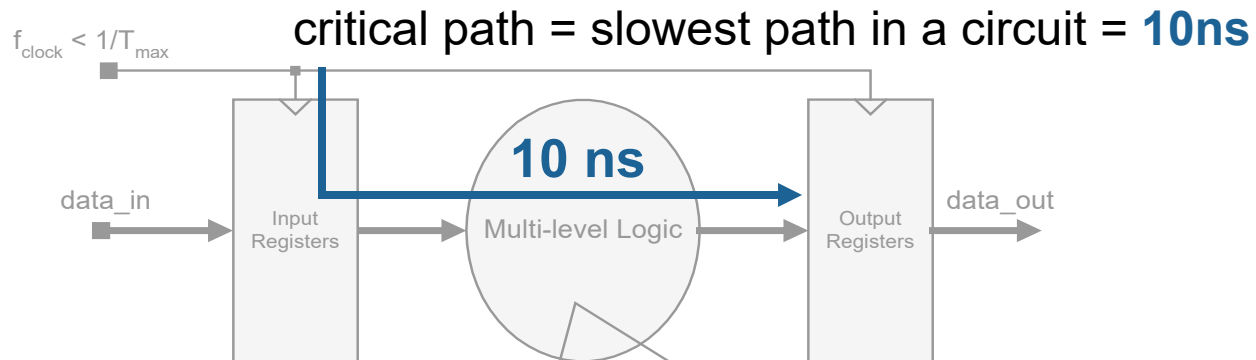

❖ 2-stage pipelining

 





Example: A Simple Circuit

❖ Original

```
always @ (posedge clk) begin
    compare <= A ~^ B;
    result  <= A + B + C + D;
end
```

❖ 3-stage pipelining

  
```
always @ (posedge clk) begin
    stage1_1 <= A ~^ B;
    stage1_2 <= A + B;
    stage1_3 <= C;
    stage1_4 <= D;
    stage2_1 <= stage1_1;
    stage2_2 <= stage1_2 + stage1_3;
    stage2_3 <= stage1_3;
    compare  <= stage2_1;
    result   <= stage2_2 + stage2_3;
end
```






Example: Pipelined 16-bit Adder

❖ Original

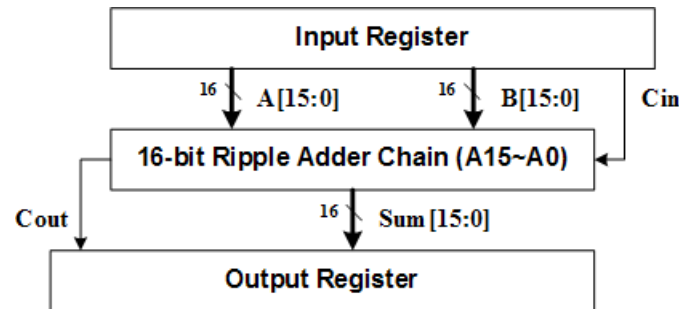

❖ 2-stage pipelining

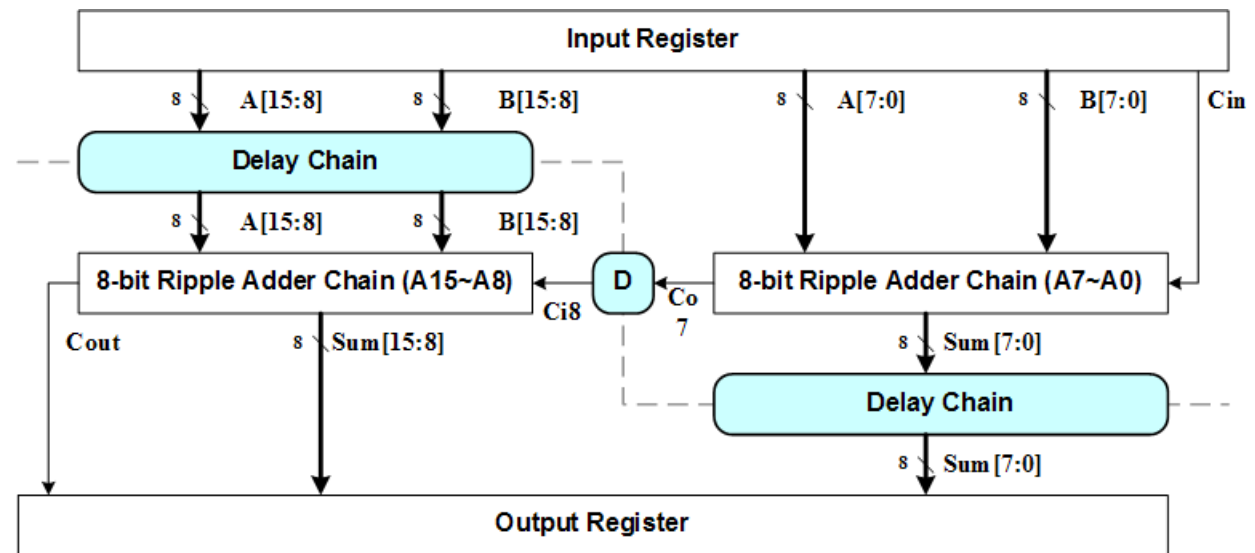




Example: FIR Filter

❖ Original

$$w(n) = ax(n) + bx(n-1)$$

$$y(n) = cx(n-2) + w(n)$$

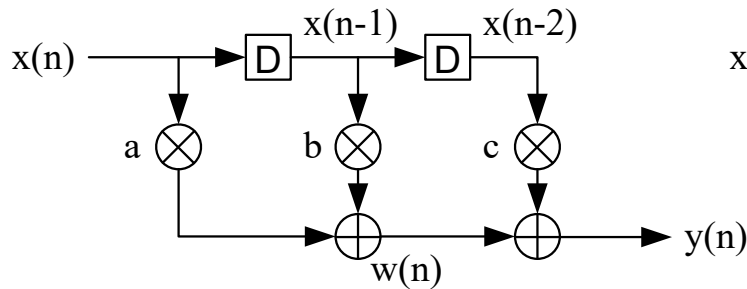


$$\text{critical path} = T_{\text{MUL}} + 2T_{\text{ADD}}$$

❖ 2-stage pipelining

$$w(n-1) = ax(n-1) + bx(n-2)$$

$$y(n-1) = cx(n-3) + w(n-1)$$

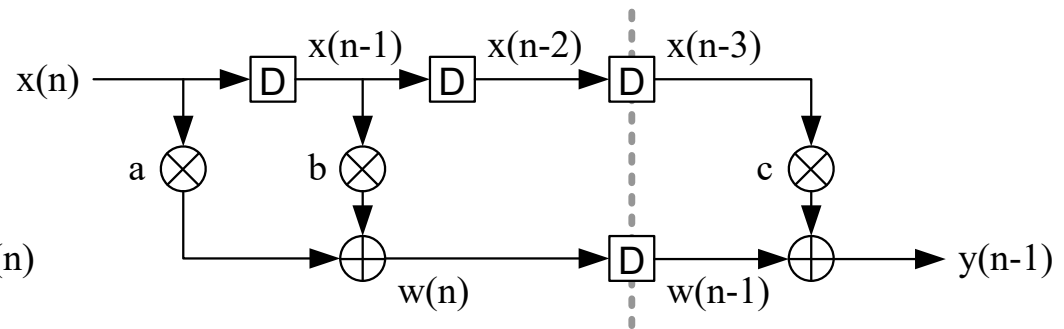

$$\text{critical path} = T_{\text{MUL}} + T_{\text{ADD}}$$




Pipelining a Design

- ❖ Draw the circuit diagram as a **directed graph**
- ❖ Put pipeline registers on **feed-forward cutset** of the graph
 - **Cutset**: a set of edges such that if they are removed from the graph, the graph becomes two disjoint sets
 - **Feed-forward**: all the edges have the **same direction** from one disjoint set to the other
- ❖ A **pipeline cutset** is a feed-forward cutset and **all inputs and outputs are in different disjoint sets**




Feed-Forward Cutset

 




Balancing Performance between Stages

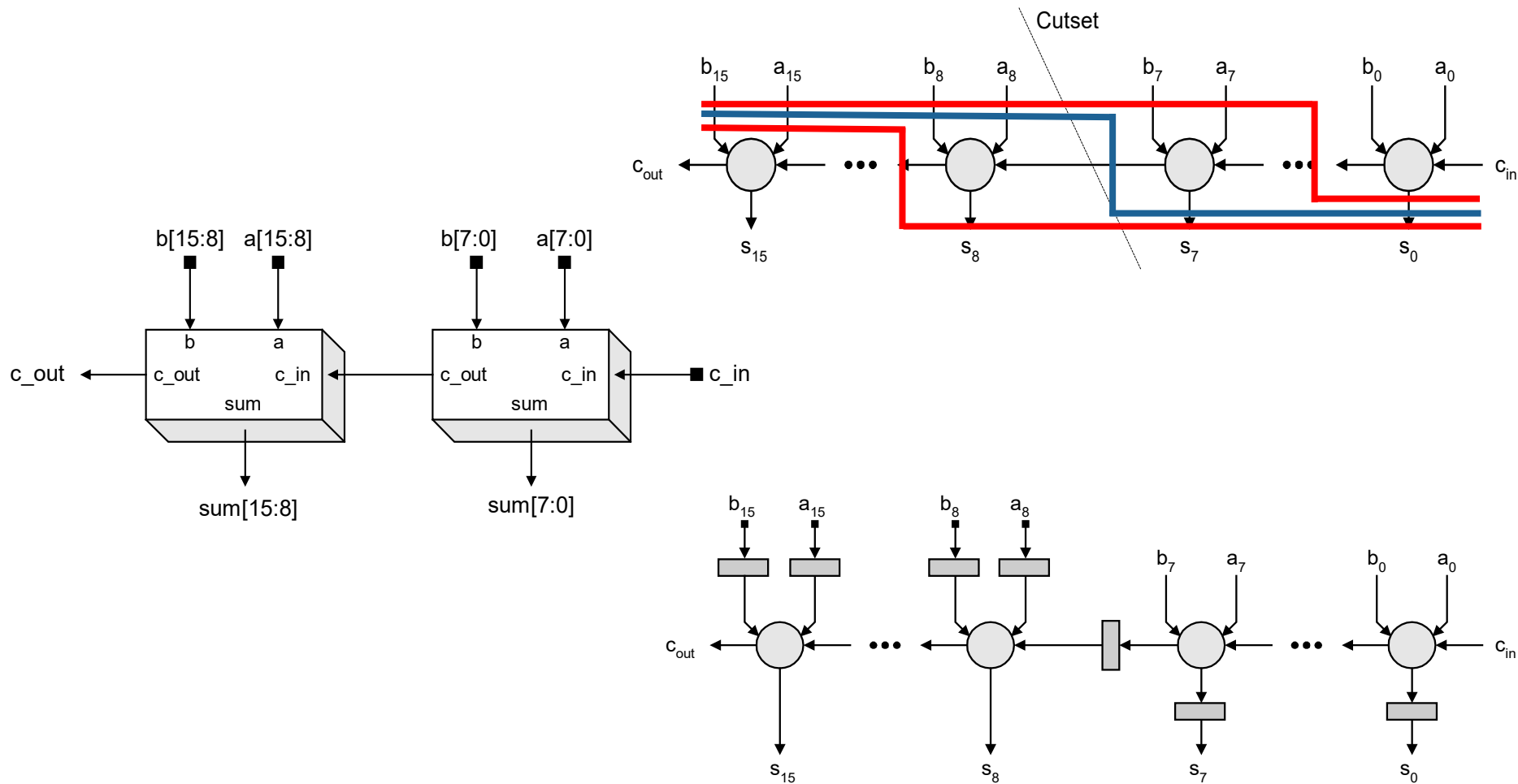



Example: Pipelined 16-bit Adder

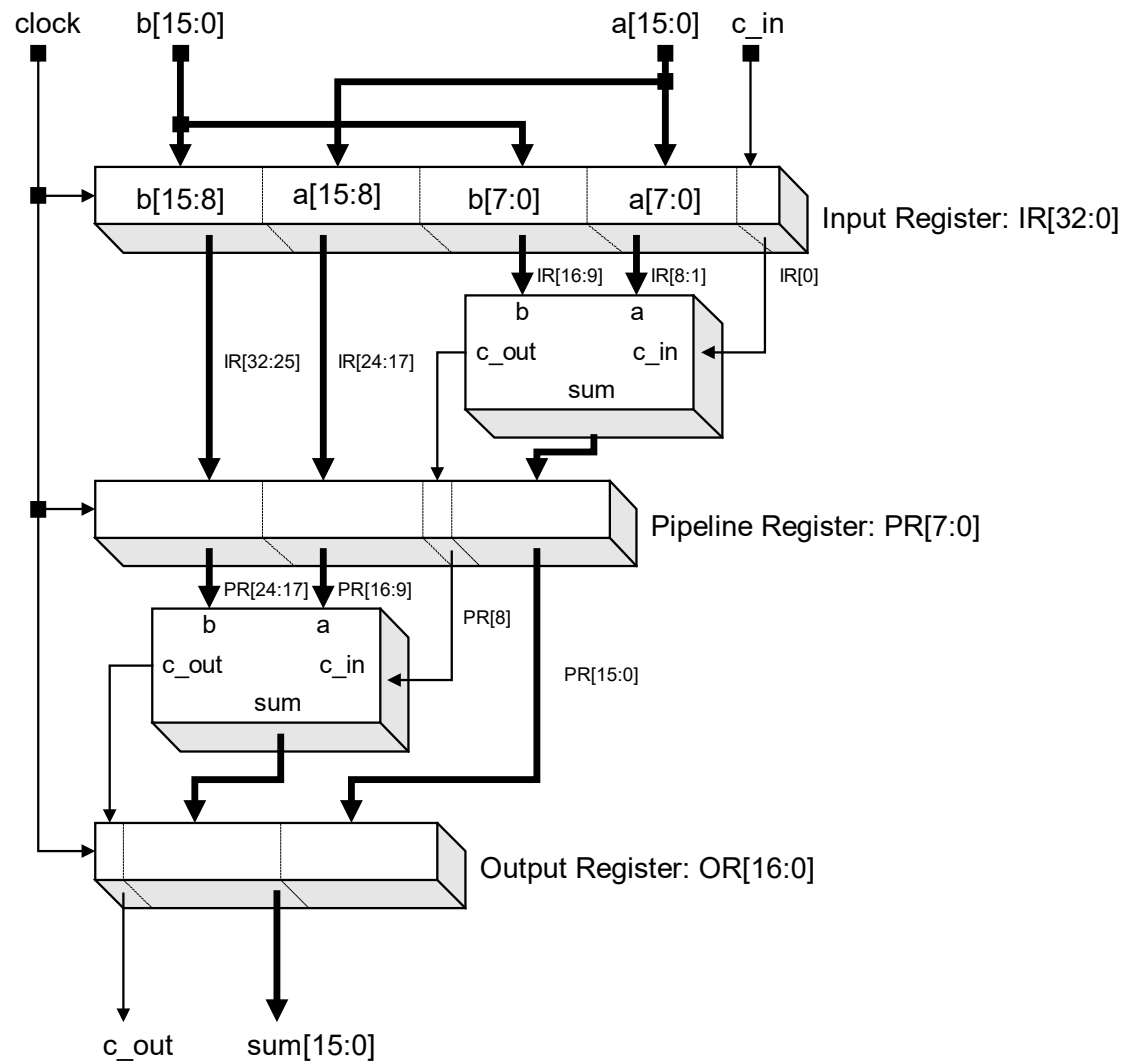



Pipeline Overhead

- ❖ **Area overhead** from pipeline registers
- ❖ **Latency overhead** from pipeline registers
 - N-stage pipeline registers -> N-cycle latency
- ❖ Some additional overhead
 - Register setup time
 - Non-ideal separation-> not exactly $1/N$ period
- ❖ **Retiming** for more balanced pipeline stage separation



Outline

- ❖ Introduction
- ❖ Register Timing
- ❖ Timing Improvements
 - Pipeline
 - Retiming
 - Parallel
- ❖ Area and Power



Retiming (1/2)

❖ Changing location of registers without affecting functionality

- Balance latency on different combinational path
- Possible reduction on clock period

❖ Note


- May change the number of registers in a design
- Retiming can be applied by synthesis tool




Retiming (2/2)

❖ Cutset retiming

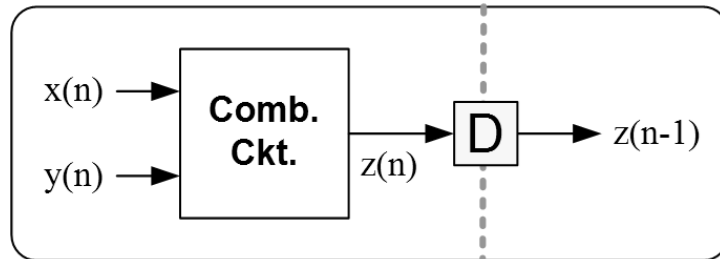- Moving/adding registers on a feed-forward cutset



1 register

 

2 registers

❖ In Design Compiler:


- `compile_ultra -retime`
(no retiming by default)



Example: Retiming (1/2)


❖ Original

Clock period > 11ns

 

❖ After Retiming

Clock period > 8ns

 




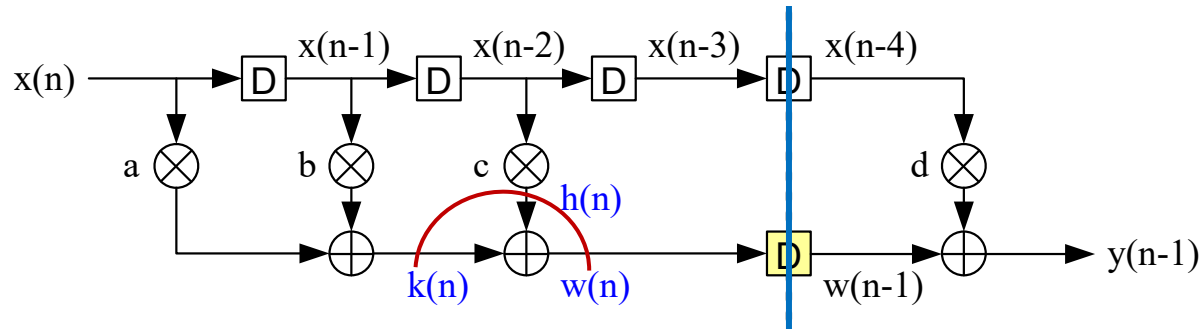Example: Retiming (2/2)


❖ Original

Clock period $> T_{\text{MUL}} + 2T_{\text{ADD}}$



❖ After Retiming

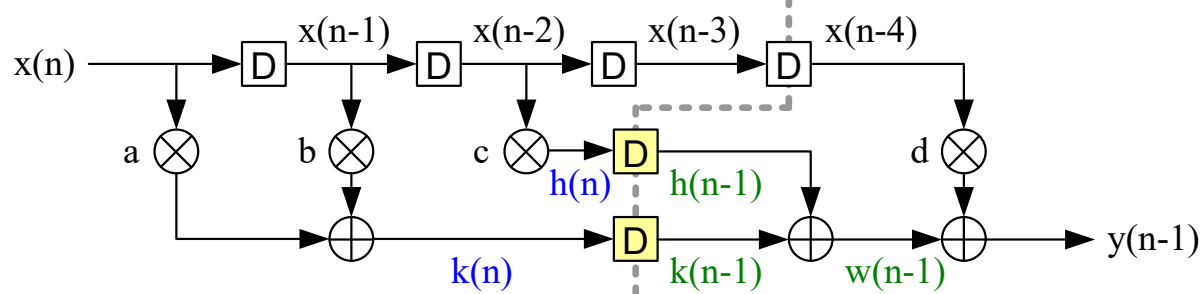Clock period $> T_{\text{MUL}} + T_{\text{ADD}}$






Outline


- ❖ Introduction
- ❖ Register Timing
- ❖ Timing Improvements
 - Pipeline
 - Retiming
 - Parallel
- ❖ Area and Power



Parallel Architecture

 


(a) reference

 

larger T_c (b) parallel

same throughput

 


(c) pipeline



Parallel Architecture: Timing

❖ For circuits with **same throughput**, parallel architecture will have:

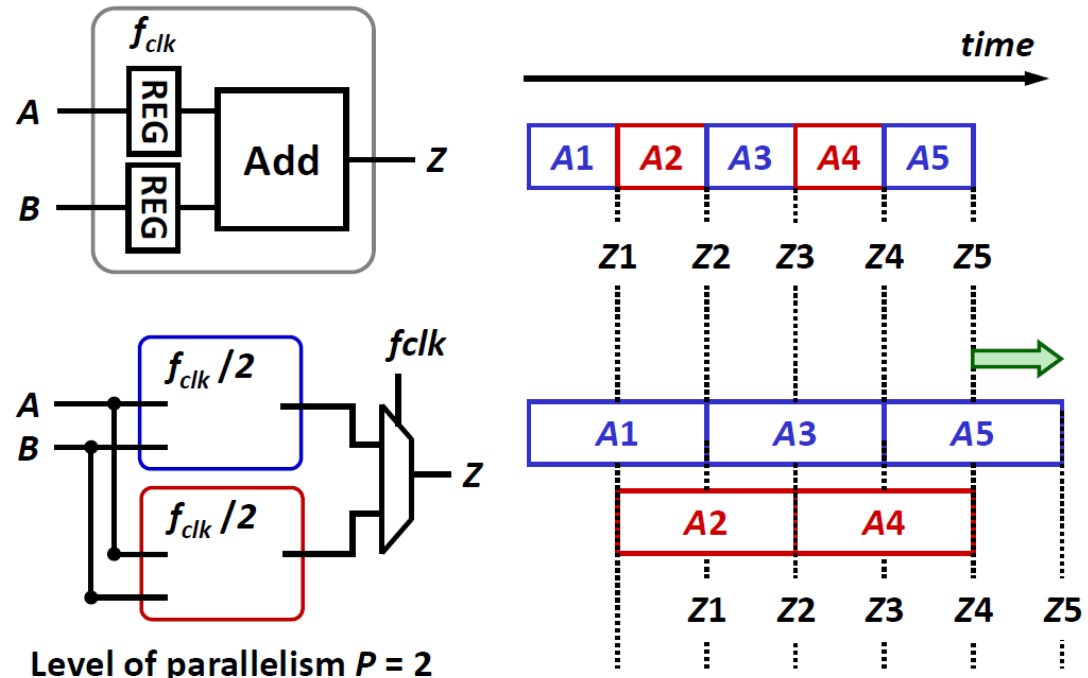
- Lower frequency
- Larger area
- Lower dynamic power
- Longer latency





Parallel Architecture: Performance

 - ❖ For circuits with **same frequency**, parallel architecture can also be used to increase performance
- ❖ Amdahl's Law: number of parallel architecture may not speed up along with parallelizing factor
 - Non-parallelizable operations
 - Dependency between data
 - Dependency between operations
 - Limitation of I/O bottleneck (communication bounded)





Outline

- ❖ Introduction
- ❖ Register Timing
- ❖ Timing Improvements
 - Pipeline
 - Retiming
 - Parallel
- ❖ Area and Power



Area Issues

❖ Area is cost

- During design process, designers should be aware of area
- Basic approach: hardware sharing

```
wire [15:0] A, B, C;  
wire [ 7:0] P, Q, R;  
wire      mult_sel;  
  
assign A = P * Q;  
assign B = P * R;  
assign C = mult_sel ? A : B;
```





```
wire [15:0] C;  
wire [ 7:0] P, Q, R, S;  
wire      mult_sel;  
  
assign S = mult_sel ? Q : R;  
assign C = P * S;
```

❖ There are tradeoffs between area and timing

- Can be specified in synthesis constraints



Power Issues

  

- ❖ Low power design is more important in modern chips due to heat dissipation, packaging, and portability requirements



Dynamic Power in CMOS

$$\text{Dynamic power, } P = \sum \alpha C V_{dd}^2 f$$

- ❖ α : switching activity
- ❖ f : clock frequency
- ❖ C : node capacitance
- ❖ V_{dd} : power supply voltage



Strategies for Low Power Design

❖ Reducing Clock Frequency

- Slower clock in power saving mode
- Lower frequency with **voltage scaling**

❖ Reducing Switching Activity

- Avoid unnecessary circuit switching
- Reducing switching activity at I/O pins
- **Clock gating**


- ❖ **Note:** these techniques can reduce dynamic power, but in modern technologies, leakage power is also important




Voltage Scaling

❖ Assume maintaining the same throughput

— **Pipelining:**

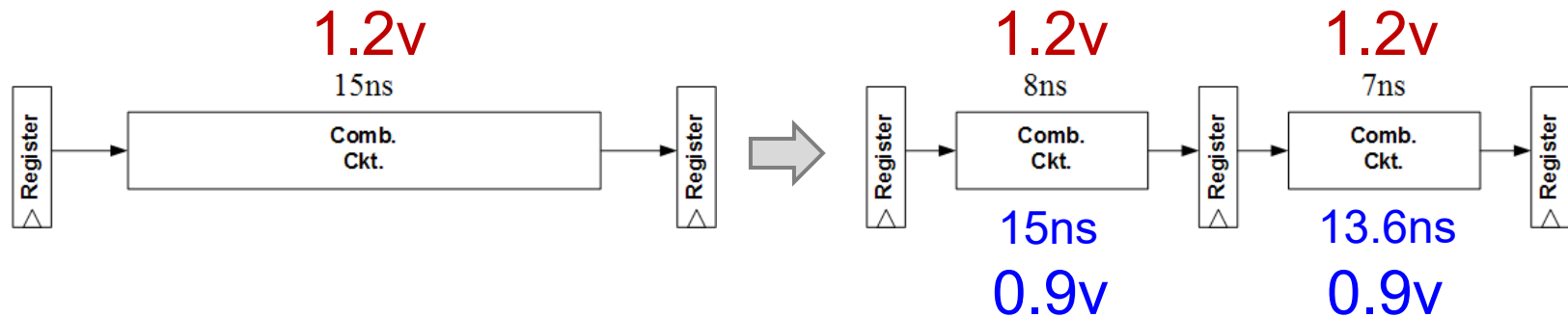


— **Parallelizing:**

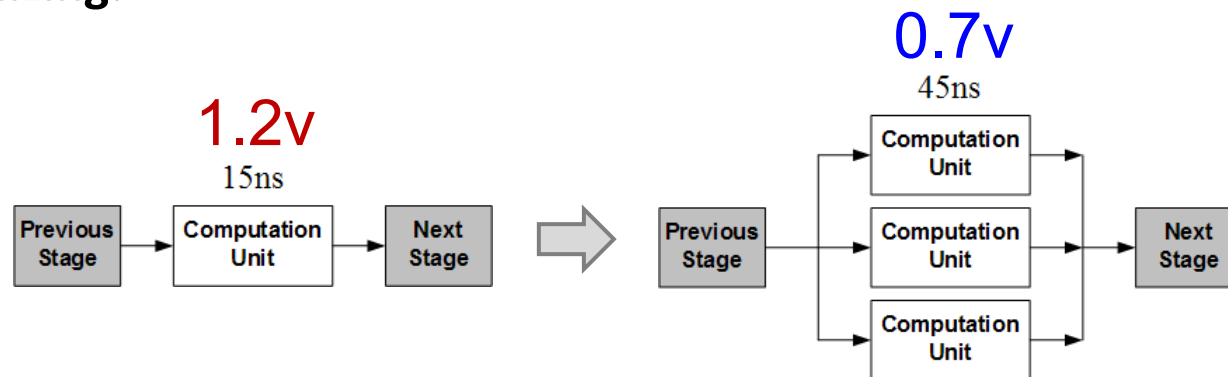



 
Example: Input Isolation for Multiplier

```
reg [31:0] C;  
reg [15:0] A, B;  
  
always @ (posedge clk) begin  
    C <= A * B;  
end
```



Gated
 
```
reg [31:0] C;  
reg [15:0] A, B;  
wire [15:0] A_, B_;  
assign A_ = gate ? 0 : A;  
assign B_ = gate ? 0 : B;  
  
always @ (posedge clk) begin  
    C = A_ * B_;  
end
```



Computer-Aided VLSI System Design

Chap.4-2 Digital Design Guidelines: From Specification to Circuit

Lecturer: 孫振庭 (Brian)

Graduate Institute of Electronics Engineering, National Taiwan University



NTU GIEE



Outline

- ❖ Design Planning
- ❖ Design Structure
- ❖ Finite State Machines
- ❖ More on Debugging
- ❖ Tools for Design Planning



Planning Your Design

1. Specifications

- Module interface
- Timing diagram
- Control flow and protocol

2. Control Flow

- Design a finite state machine (FSM)
- Determine transition conditions
- Determine state outputs

3. Datapath


4. Others

- Reset strategy (sync/async, active high/low)
- Verify on paper before coding



Datasheet & Timing Diagram

 - ❖ At the beginning of digital circuit design:
 - I/O specification: bit width, active high/low, input/output, ...
 - Timing specification: operating frequency, input/output delay, ...
- ❖ Example: documenting the signals of your design




信號名稱	輸/出入	位元寬度	說明
<i>reset</i>	input	1	高位準非同步(active high asynchronous)之系統重置信號。 說明:本信號應於系統啟動時送出。
<i>clk</i>	input	1	時脈信號。 說明:此系統為同步於時脈正緣(posedge)之同步設計。
<i>cmd</i>	input	4	指令輸入信號。 說明:本控制器共有九種指令輸入,相關指令說明請參考表二。指令輸入只有在 <i>cmd_valid</i> 為 high 及 <i>busy</i> 為 low 時,為有效指令。
<i>cmd_valid</i>	input	1	有效指令輸入信號。 說明:當本信號為 high 時表示 <i>cmd</i> 指令為有效指令輸入。
<i>datain</i>	input	8	八位元影像資料輸入埠。
<i>dataout</i>	output	8	八位元影像資料輸出埠。
<i>output_valid</i>	output	1	有效資料輸出信號。 說明:當本信號為 high 時表示 <i>dataout</i> 為有效資料輸出。
<i>busy</i>	output	1	系統忙碌信號。 說明:當本信號為 high 時,表示此控制器正在執行現行(current)指令,而無法接收其他新的指令輸入。




Example: SRAM (1/2)

- ❖ Control address for data read
- ❖ Control address, input data, write enable for data write

Read timing

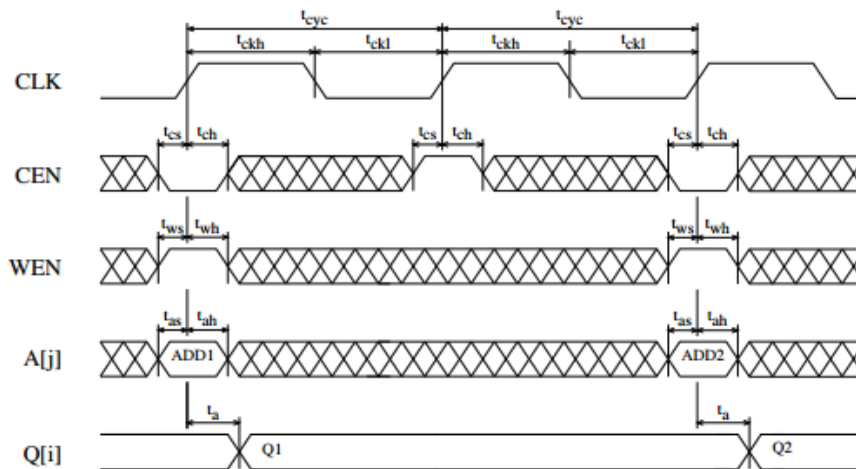

Write timing

 





Example: SRAM (2/2)

- ❖ Control address for data read
- ❖ Control address, input data, write enable for data write
- ❖ Draw timing diagrams for sequential circuits based on specs

Read timing

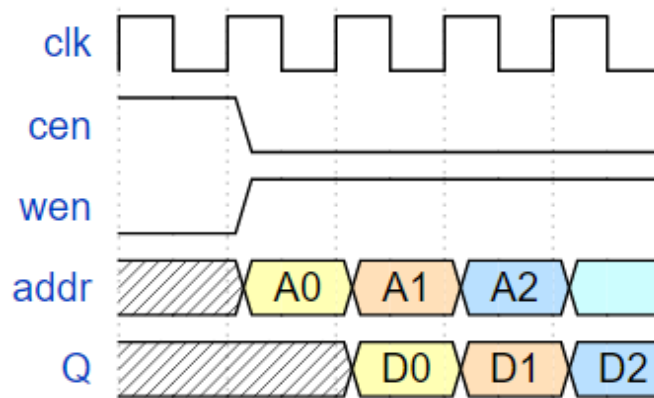

Write timing

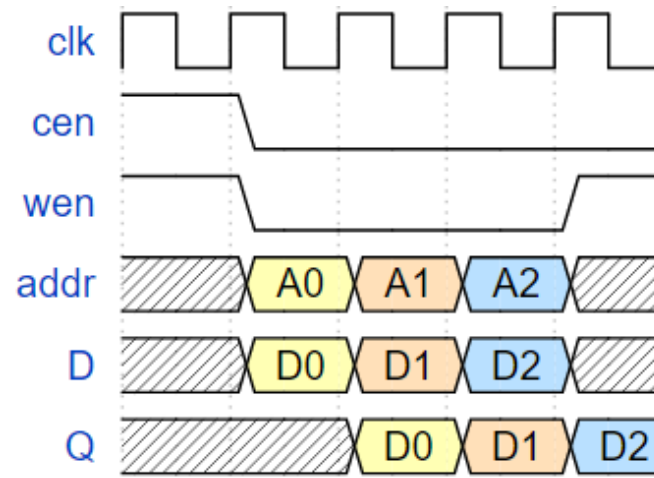



Reset Strategy

- ❖ Reset is a global signal distributed across the entire chip
- ❖ Initialize the chip to the idle state
- ❖ Be aware of reset behavior
 - Timing: synchronous/asynchronous
 - Trigger: active low/active high

```
always @ (posedge clk or negedge rst_n) begin
    if (~rst_n) begin
        // Reset assignment
    end
    else begin
        // Next state assignment
    end
end
```

Asynchronous active-low reset

```
always @ (posedge clk) begin
    if (rst) begin
        // Reset assignment
    end
    else begin
        // Next state assignment
    end
end
```

Synchronous active-high reset



Outline

- ❖ Design Planning
- ❖ Design Structure
- ❖ Finite State Machines
- ❖ More on Debugging
- ❖ Tools for Design Planning



Controller & Datapath (1/2)

❖ Separate controller and datapath

❖ **Controller**

- Controls the operations of datapath modules
- e.g.: **FSM**, counter

❖ **Datapath**

- Performs computation with the input data
- e.g. arithmetic & logic units, data registers, MUX




Controller & Datapath (2/2)

❖ Control signals

- Determine the detailed operations to be performed on the datapath
- e.g.: FSM states, start, select signals

❖ Status signals

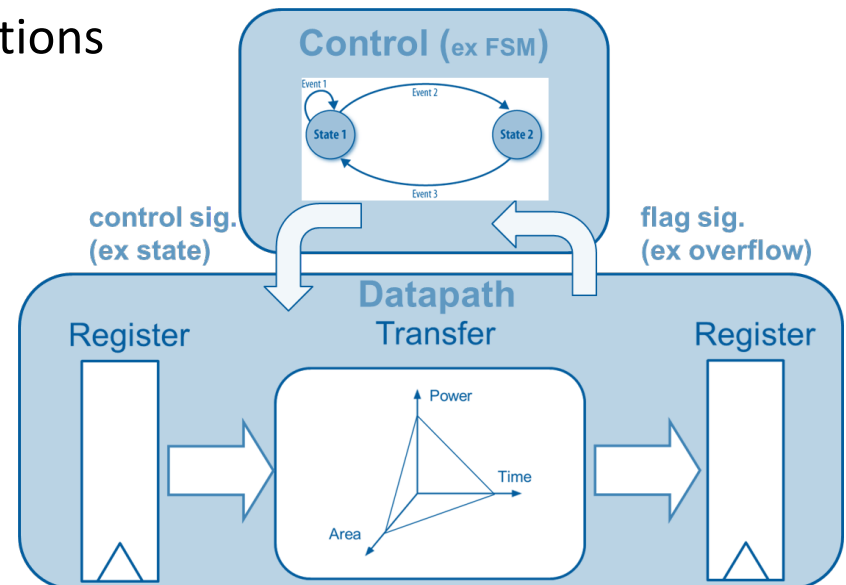
- Indicate the status of datapath modules
- e.g. flags, finish, overflow, exceptions






Control Strategy

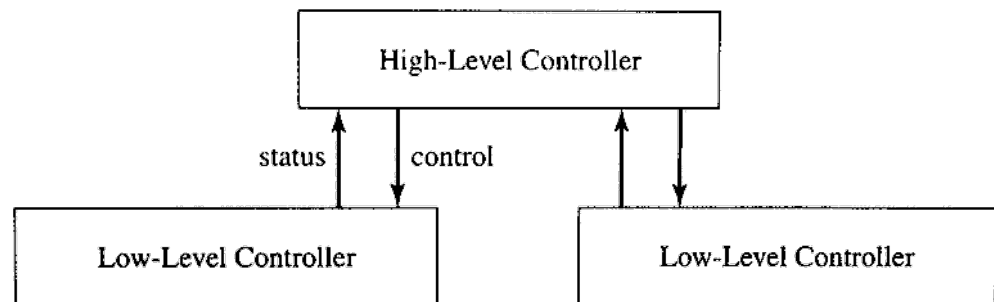- ❖ **Make sure the behavior of control signals are correct**
- ❖ Generally, control sequence are generated by one or a combination of the following strategies:
 - **Finite state machines (FSMs)**
 - Top-down controllers
 - Counters
 - Software



Hierarchical Control (preferred)

 

Interconnected Control (discouraged)




Structuring the Datapath

- ❖ Begin with block diagrams
- ❖ Determine the functional units and their connection
 - Low-level instances (e.g. arithmetic, logic)
 - Memory instances (SRAM)
 - Submodules
- ❖ Determine the design strategy
 - Pipelining stages
 - Parallelization degree



Datapath Design (1/3)

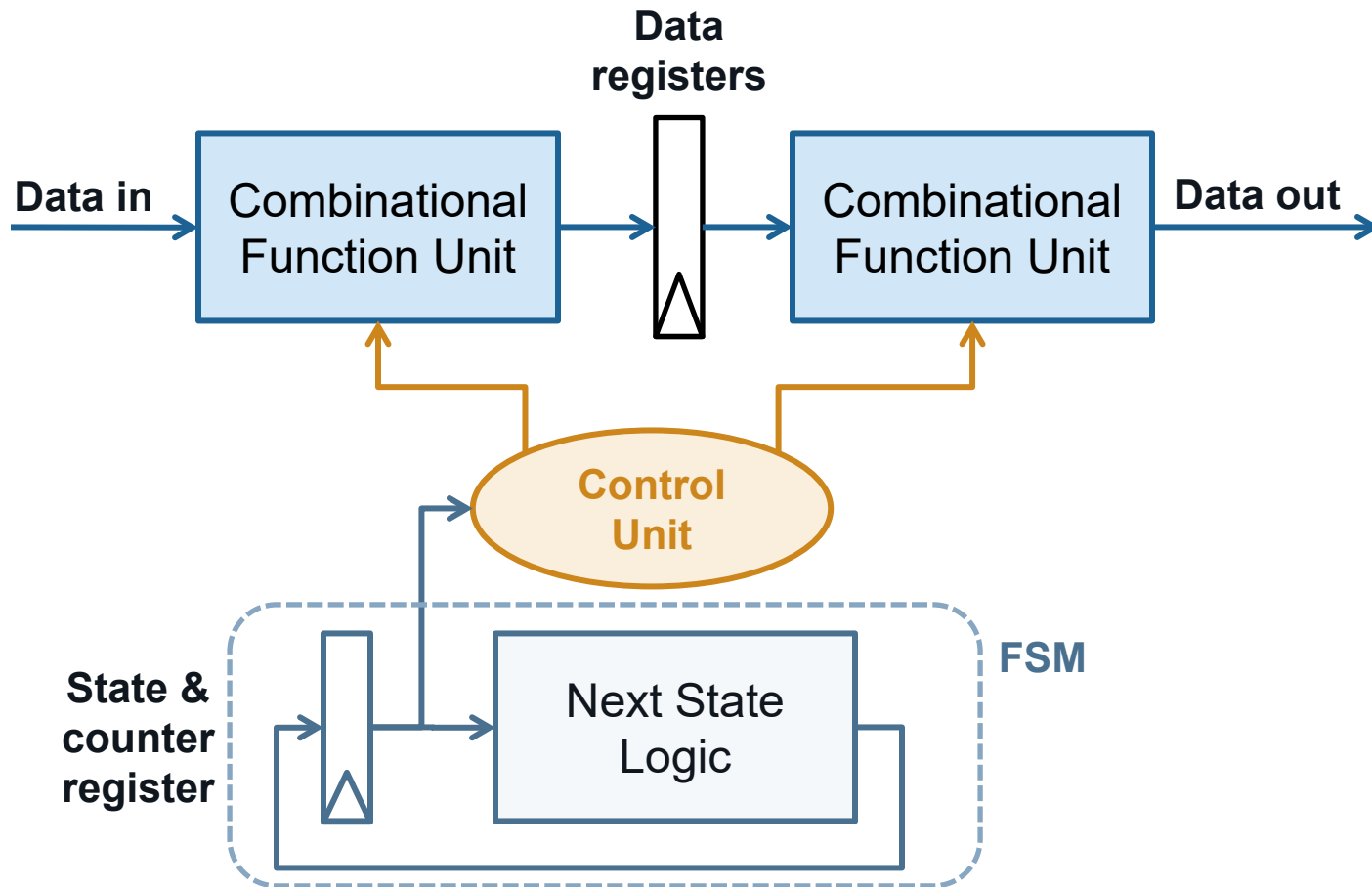





Datapath Design (2/3)

❖ Pipeline

- Gain throughput & clock speed

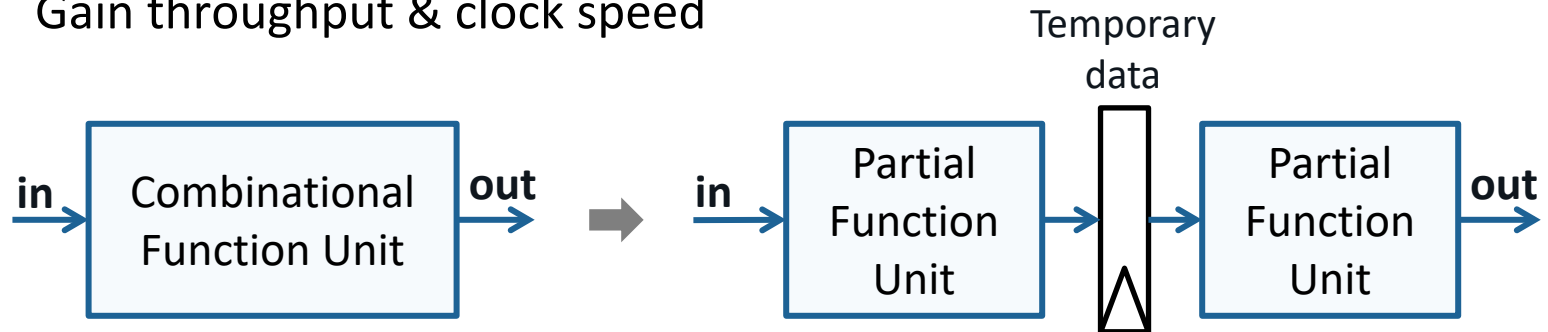

- Feedback loops cannot be pipelined

 





Datapath Design (3/3)

❖ Functional block reusing

- Reduce combinational area

 

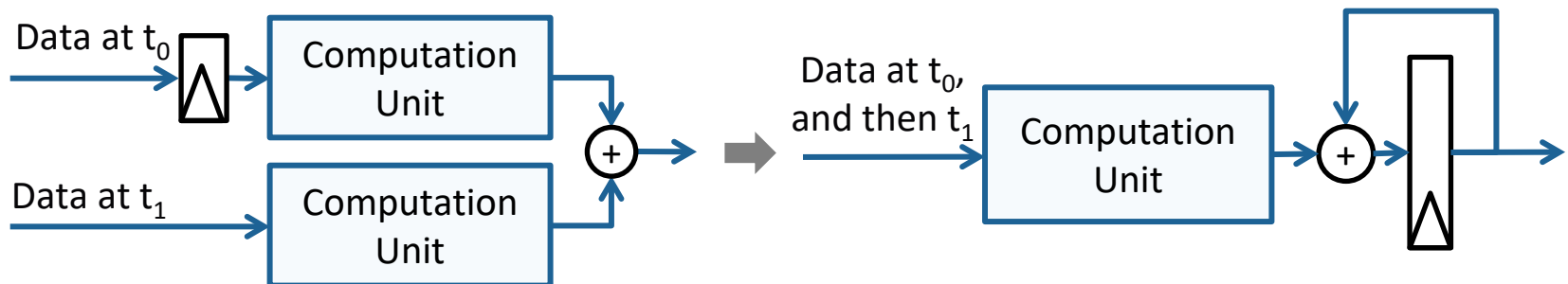
- Reduce area when input comes sequentially






Note: Verify before Coding

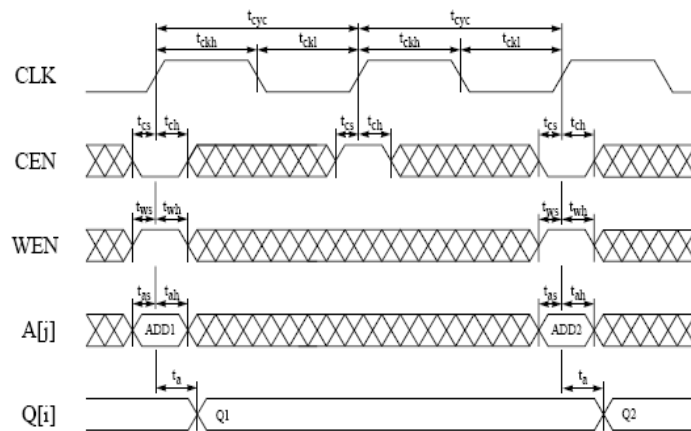- ❖ It is a useful practice to hand-simulate the design before coding
- ❖ Draw a timing diagram capturing critical events (e.g. state transitions and signal changes)



specification

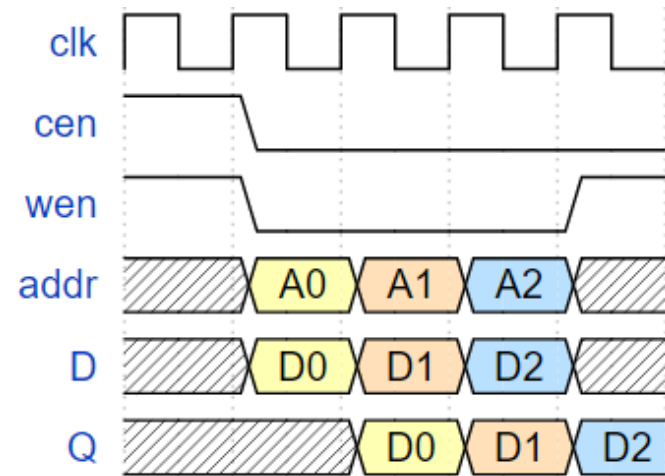

timing in your design



Conclusion: Partition for Synthesis

- ❖ Separate combinational and sequential logic (Chap. 3)
- ❖ Separate control and datapath (Chap. 4-2)
- ❖ Register at hierarchical output (Chap. 3)

- ❖ Keep major blocks separated (draw block diagrams)
- ❖ Avoid glue logic (logic between module connections)
- ❖ Avoid asynchronous logic, false path, and multi-cycle path



Outline

- ❖ Design Planning
- ❖ Design Structure
- ❖ Finite State Machines
- ❖ More on Debugging
- ❖ Tools for Design Planning



Finite State Machines (FSMs)


- ❖ An abstract machine that can be in exactly one of a finite number of states at any given time
 - **Input:** data fed into the machine
 - **Transition:** state change based on current state and input
 - **Output:** data output based on current state and/or input

- ❖ **Types of FSMs**
 - **Mealy:** output determined by **its current state** and **inputs**
 - **Moore:** output determined only by **its current state**




Mealy and Moore FSM (1/2)

Mealy

 


Moore

 




Mealy and Moore FSM (2/2)

❖ Mealy (combinational output)

 

❖ Moore (sequential output)

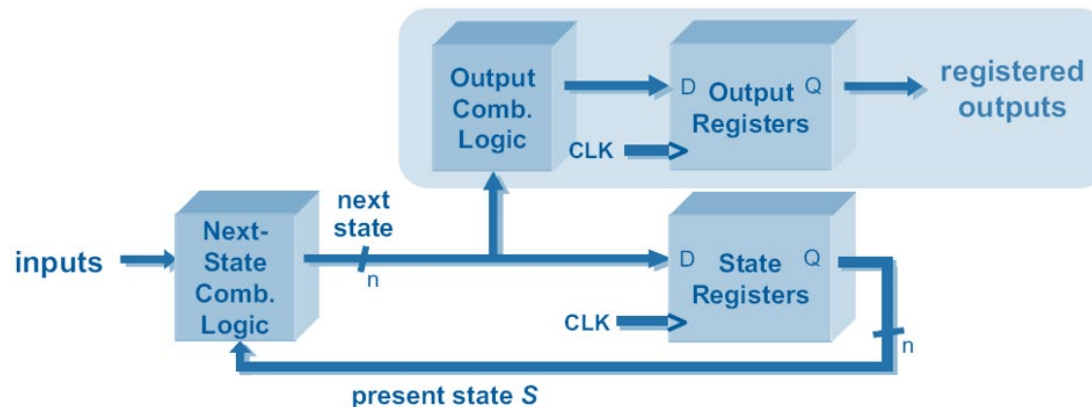



Example: FSM in Verilog

```
localparam S_IDLE = 2'd0;  
localparam S_READ = 2'd1;  
localparam S_WRITE = 2'd2;  
localparam S_DONE = 2'd3;
```

Use localparam or enum
for state constants

```
reg [1:0] state_r, state_w;
```

State register

```
always @ (*) begin  
    state_w = state_r;  
    case (state_r)  
        S_IDLE: begin ... end  
        S_READ: begin ... end  
        S_WRITE: begin ... end  
        S_DONE: begin ... end  
    endcase  
end
```


State transitions

```
always @ (posedge clk or posedge  
rst) begin  
    if (rst) begin  
        state_r <= S_IDLE;  
    end  
    else begin  
        state_r <= state_w;  
    end  
end
```



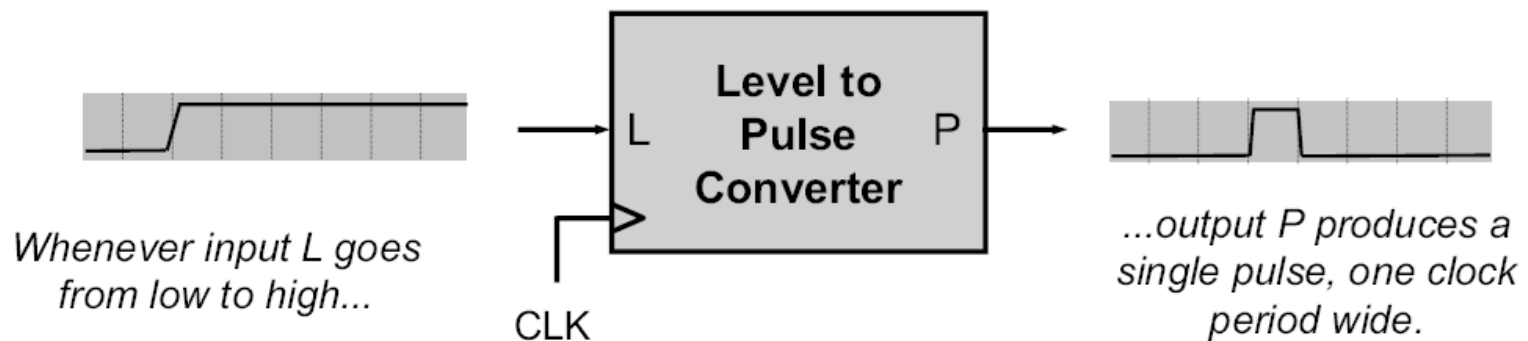
Example: Level-to-Pulse Converter (1/2)

- ❖ Produces a single-cycle pulse every time when input goes from low to high
 - e.g. a synchronous rising edge detector
- ❖ Applications
 - Button and switches
 - Single-cycle enable signal







Example: Level-to-Pulse Converter (2/2)

 

- Since outputs are determined by state *and* inputs, Mealy FSMs may need fewer states than Moore FSM implementations

  1. When $L=1$ and $S=0$, this output is asserted **immediately** and **until** the state transition occurs (or L changes).



Output transitions immediately.
State transitions at the clock edge.



Outline

- ❖ Design Planning
- ❖ Design Structure
- ❖ Finite State Machines
- ❖ **More on Debugging**
- ❖ Tools for Design Planning



RTL Debugging


❖ Tracing signals

- When *S* is incorrect, check what drives *S* first
- Backward trace until the error source is found
- Tool: nTrace

❖ Check control signals first

- FSM state transitions
- Start/done, valid/ready handshake signals

❖ Note: Partial vector signal in nWave


 




Naming Conventions for Debugging

- ❖ Use suffix in signal naming to show the attributes of signals
 - signal_n: active-low
 - signal_w: wire
 - signal_r: register
 - signal_next: next FSM state
 - signal_cur: current FSM state

- ❖ Alphabetical naming for debugging

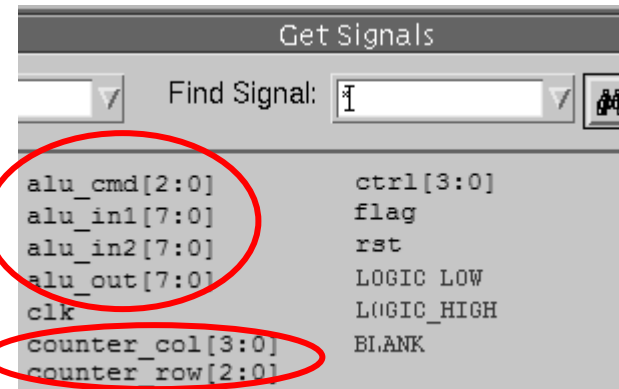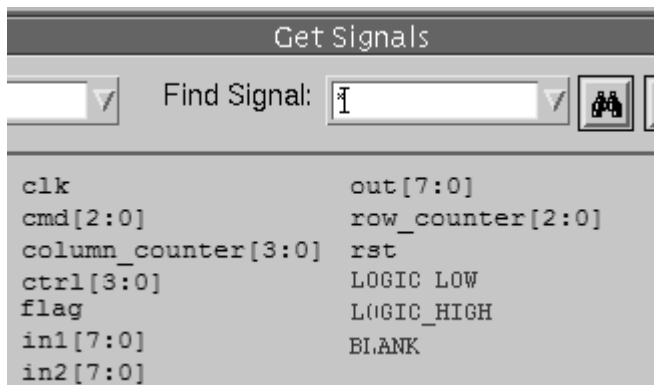



Timing Checks in Post-Synthesis Simulation (1/2)

❖ SDF annotation

- Make sure that the SDF file exists, and the path is correct
 - Make sure that the SDF file is parsed correctly during simulation
- ```
$sdf_annotate("design.sdf", testbench)
```

## ❖ Input delay and output delay

- Synthesis tool does not know when the inputs come, and when the outputs are captured
- Default: No input and output delay during synthesis
- Set the constraints properly (Chap. 5)
- Model input and output delay correctly in testbench





# Timing Checks in Post-Synthesis Simulation (2/2)

## ❖ Setup-time violation

- Input of flip-flop not state during clock trigger
  - Unexpected long combinational delay
  - Combinational loop
  - Improper input delay constraints

## ❖ Hold-time violation

- Should be fixed in place-and-route stage (insert buffers)

- ❖ Also check if the timing violations are caused by the reset signal, which can be fixed by using correct reset timing




# Outline

- ❖ Design Planning
- ❖ Design Structure
- ❖ Finite State Machines
- ❖ More on Debugging
- ❖ Tools for Design Planning


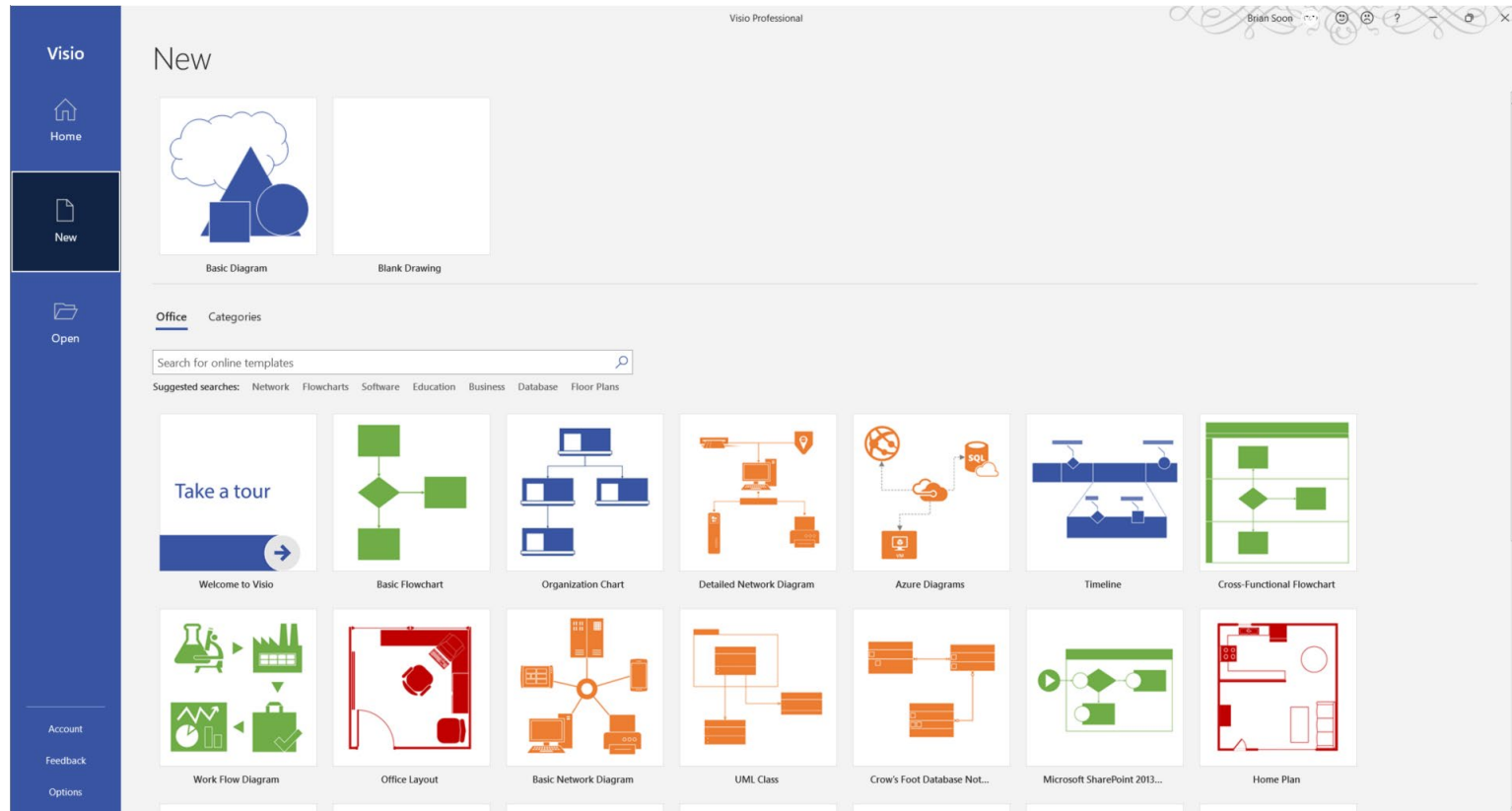
# Block Diagram: Microsoft Visio


❖ A powerful tool for block diagram and flowchart




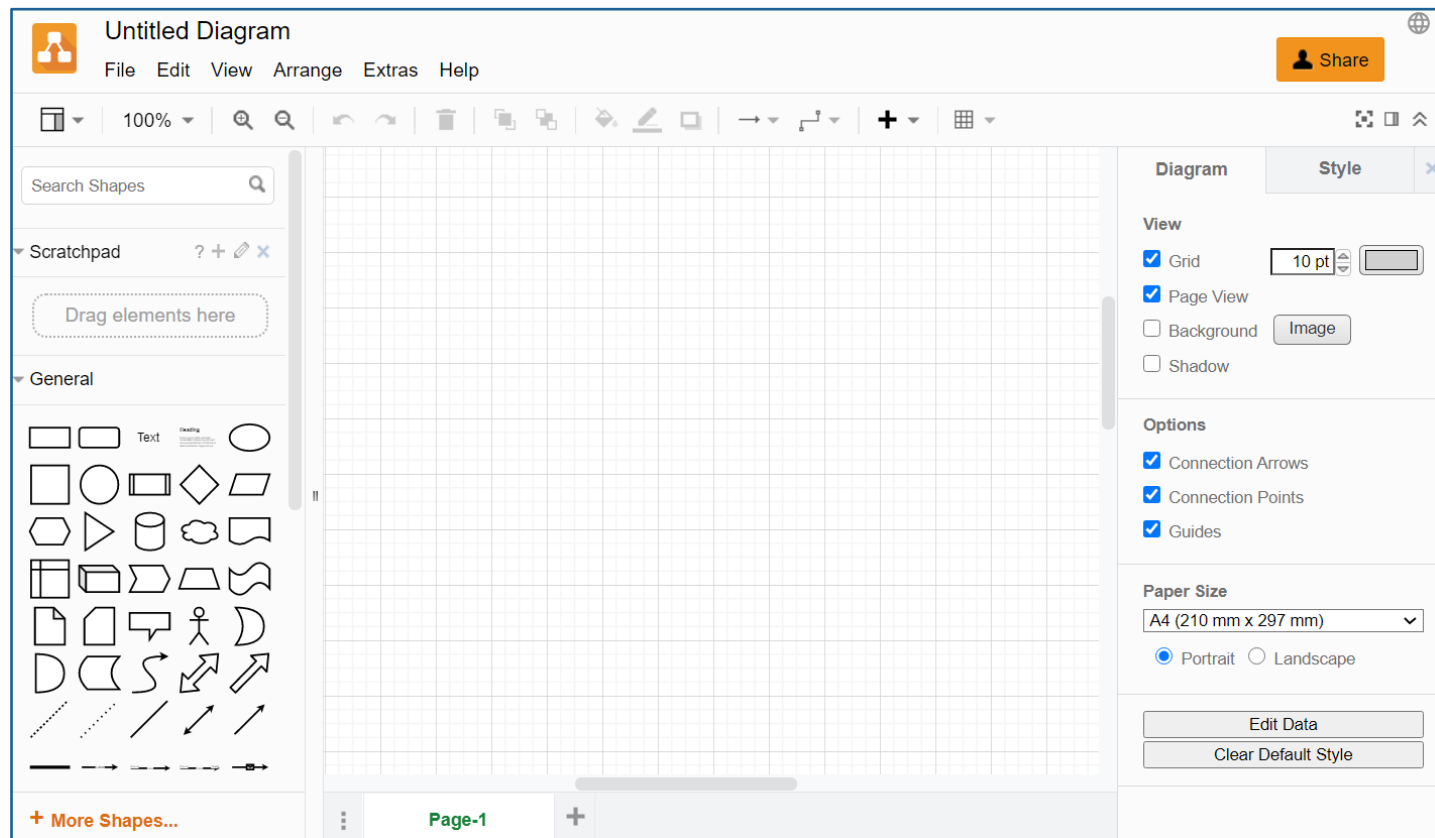
# Block Diagram: draw.io

- ❖ An open-source diagram software
- ❖ Website: <https://app.diagrams.net/>






# Timing Diagram: WaveDrom

- ❖ An open-source timing diagram software
- ❖ Website: <https://wavedrom.com/>

```
{ signal: [
 { name: "clk", wave: "p.....|..." },
 { name: "Data", wave: "x.345x|=.x",
 data: ["head", "body", "tail", "data"] },
 { name: "Request", wave: "0.1..0|1.0" },
 {},
 { name: "Acknowledge", wave: "1.....|01." }
]}
```

 




# FSM: LaTeX + TikZ

```

\documentclass{article}

\usepackage{tikz}
\usetikzlibrary{automata,positioning}
\begin{document}
\begin{tikzpicture}[shorten >=1pt,node distance=2cm,on grid,auto]
 \node[state,initial] (q_0) {q_0};
 \node[state] (q_1) [above right=of q_0] {q_1};
 \node[state] (q_2) [below right=of q_0] {q_2};
 \node[state,accepting] (q_3) [below right=of q_1] {q_3};
 \path[->]
 (q_0) edge node {0} (q_1)
 edge node [swap] {1} (q_2)
 (q_1) edge node {1} (q_3)
 edge [loop above] node {0} ()
 (q_2) edge node [swap] {0} (q_3)
 edge [loop below] node {1} ();
\end{tikzpicture}
\end{document}

```

 



# Visual Studio Code Integration

The screenshot displays the Visual Studio Code interface with three integrated extensions highlighted by red boxes:

- LaTeX**: The `fsm.tex` file is open, showing LaTeX code for a finite state machine diagram. The code includes `\documentclass{article}`, `\usepackage{tikz}`, and `\usetikzlibrary{automata,positioning}`. It defines four states: `q_0` (initial), `q_1`, `q_2`, and `q_3` (accepting). Transitions are defined between these states.
- WaveDrom**: The `test.json` file is open, showing a JSON configuration for a waveform. It defines signals: `clk` (clock), `Data` (data bus), `Request`, and `Acknowledge`. The `Data` signal is configured with a specific waveform pattern.
- Draw.io**: The `test.drawio` file is open, showing a block diagram. The diagram includes a `Control` block, a `Decoder` block, a `Data path` block, and four `SRAM` blocks (`SRAM0`, `SRAM1`, `SRAM2`, `SRAM3`). The `Control` block is connected to the `Decoder` block, which in turn connects to the `Data path` block. The `Data path` block is connected to the four `SRAM` blocks.

The bottom status bar shows the current position: Ln 2, Col 1, Spaces: 4, UTF-8, CRLF, LaTeX.

Extensions: LaTeX Workshop, Draw.io Integration, Waveform Render